

K Prasanna Kumar and G V V Sharma

## CONTENTS

<b>1</b>	<b>Installation of Latex Package</b>	<b>1</b>
<b>2</b>	<b>Analog Circuits</b>	<b>1</b>
2.1	Current Measurement Circuit	1
2.2	Voltage Measurement Circuit	2
2.3	RLC Circuit . . . . .	2
2.4	Half Wave Rectifier Circuit .	2
<b>3</b>	<b>Digital Circuits</b>	<b>3</b>
3.1	Basic Gates . . . . .	3
3.2	Logic Circuit . . . . .	3
<b>4</b>	<b>FET Transistor Logic</b>	<b>3</b>
<b>5</b>	<b>Signal Flow Graph</b>	<b>4</b>
<b>6</b>	<b>Control System</b>	<b>4</b>
<b>References</b>		<b>4</b>

*Abstract*—This module explains how to draw electrical circuits using latex.

## 1 INSTALLATION OF LATEX PACKAGE

*Installation of all packages at once*

```
sudo apt-get install texlive-full
```

*Installation or Loading of individual packages*

For installing or updating particular package of texlive, we should go with following commands. In the module we make use of 'circuitikz' package, so the following helps to install or load 'circuitikz' into texlive.

The authors are with the Department of Electrical Engineering, IIT, Hyderabad 502285 India 1<sup>st</sup> e-mail: kk.prassu924@gmail.com, 2<sup>nd</sup> e-mail: {gadepall}@iith.ac.in.

```
sudo apt-get install xzdec
```

**xzdec** is an texlive package manager dependency.  
Initialize LaTeX package database

```
tlmgr init-usertree
```

Install the *circuitikz* package

```
tlmgr install circuitikz
```

Thus texlive (Latex) package can be installed or loaded.

*Documentation main frame*

```
\documentclass[12pt]{article}


\usepackage{circuitikz}
\begin{document}

\end{document}
```

## 2 ANALOG CIRCUITS
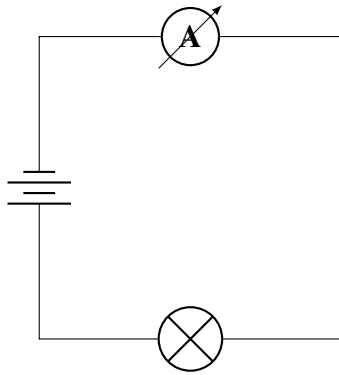
### 2.1 Current Measurement Circuit

```
\begin{center}
\begin{circuitikz} \draw
(0,0) to[battery] (0,4)
to[ammeter] (4,4) -- (4,0)
to[lamp] (0,0)
;
\end{circuitikz}
\end{center}
```




*Description ::*

- The first line "`(0,0) to[battery] (0,4)`" says that place a battery in between (0,0) & (0,4)
- The second line "`(4,4) to[battery] (4,0)`" says that place an ammeter in between (4,4) & (4,0) and Draw a line form (4,4) to (4,0)
- The third line "`(4,0) to[battery] (0,0)`" says that place lamp in between (4,0) & (0,0)
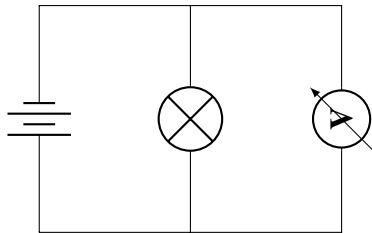
## 2.2 Voltage Measurement Circuit


```
\begin{center}
\begin{circuitikz}
\draw
(0,0) to[battery] (0,4) -- (2,4)
      to[lamp]      (2,0) -- (4,0)
      to[voltmeter] (4,4) -- (2,
                        4)
      (2,0) -- (0,0);
\end{circuitikz}
\end{center}
```



## 2.3 RLC Circuit


```
\begin{center}
\begin{circuitikz}
\draw
(0,0) to[battery] (6,0) -- (6,2)
(0,0) -- (0,2) to[R = 220 \ohm]
      (2,2) to[L = 10 mH] (4,2) to[C =
      1 F] (6,2) -- (6,0);
\end{circuitikz}
```

```
\end{center}
```

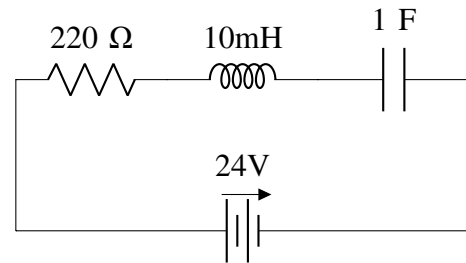


Circuit with bipoles can be drawn using above syntax. But for monopoles and multipoles the following syntax should be used
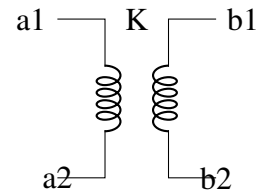
```
\begin{center}
\begin{circuitikz}
\draw
(0,0) node[transformer] (T) {}
(T.A1) node[anchor = east] {a1}
(T.A2) node(anchor = east) {a2}
(T.B1) node[anchor = west] {b1}
(T.B2) node(anchor = west) {b2}
(T.base) node{K}
;
\end{circuitikz}
\end{center}
```



## 2.4 Half Wave Rectifier Circuit


```
\begin{center}
\begin{circuitikz}
\draw
(0,2) node[transformer] (T1){}
(T1.A1) to[sinusoidal voltage
      source] (T1.A2)
(T1.B1) to[diode] (3,2) to[R]
      (3,0) |- (T1.B2)
;
\end{circuitikz}
\end{center}
```

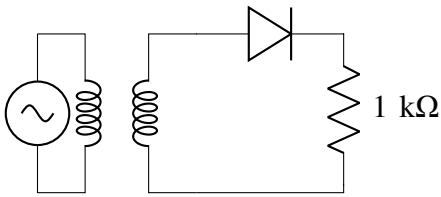

### 3 DIGITAL CIRCUITS
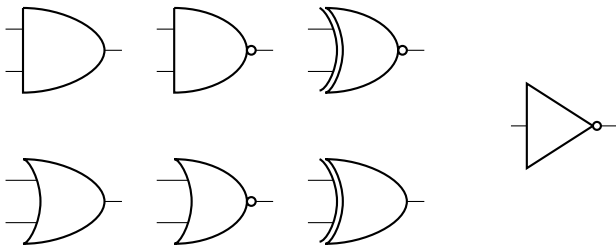
#### 3.1 Basic Gates

```
\begin{center}
\begin{circuitikz}
\draw
(4,0) node[xor port]{}
(4,2) node[xnor port]{}
(2,0) node[nor port]{}
(2,2) node[nand port]{}
(0,0) node[or port]{}
(0,2) node[and port]{}
(6,1) node[not port]{}
;
\end{circuitikz}
\end{center}
```




#### 3.2 Logic Circuit

```
\begin{center}
\begin{circuitikz}
\draw
(0,2) node[nand port] (nand4) {}
(2,3) node[nand port] (nand3) {}
(4,2) node[nand port] (nand2) {}
(0,0) node[nand port] (nand1) {}
(nand1.out) |- (nand2.in 2)
(nand4.out) |- (nand3.in 2)
(nand3.out) |- (nand2.in 1)
(nand1.in 1) node[anchor = east] {a}
(nand1.in 2) node[anchor = east] {b}
(nand3.in 1) node[anchor = east] {c}
;
```


```
(nand4.in 1) node[anchor = east] {x}
(nand4.in 2) node[anchor = east] {y}
(nand2.out) node[anchor = west] {output}
;
```

```
\end{circuitikz}
\end{center}
```

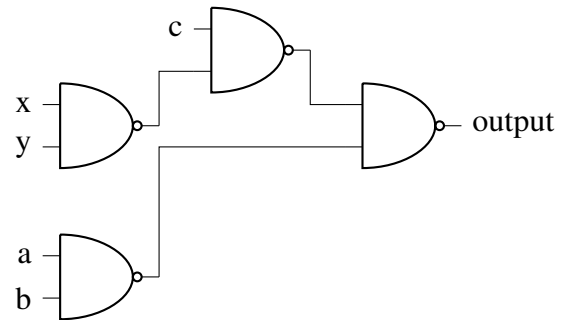

### 4 FET TRANSISTOR LOGIC

```
\begin{center}
\begin{circuitikz}
\draw
(0,3) node[pmos, emptycircle] (P1) {}
(0,1) node[nmos](N1) {}
(P1.drain) -- (N1.drain)
(P1.source) node[vcc] {5V}
(N1.source) node[ground](G) {GND}
(P1.gate) |- (N1.gate)
(-2,2) -- (-1,2) node[inputarrow] (inr1){}
(inr1.1) node[anchor = east] {A}
(0,2) -- (1,2) node[inputarrow] (inr2){}
(inr2.1) node[anchor = east] {A'}
;
\end{circuitikz}
\end{center}
```

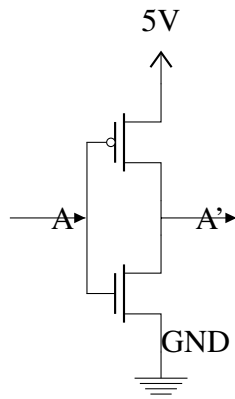

5 SIGNAL FLOW GRAPH

```


\begin{center}
\begin{circuitikz}
\draw
(0,0) to[vco] (1,0) to[adc] (3,0)
to[dsp] (5,0) to[dac] (7,0) node
[txantenna] {TX}
(1.5,-3.5) to[dac] (3.25,-3.5) to[
dsp] (5,-3.5) to[adc] (6.5,-3.5)
node[rxantenna] {RX}
(1.5,-3.5) node[inputarrow,
rotate = 180] (inr) {}
(inr.1) node[anchor = east] {
output}
;
\end{circuitikz}
\end{center}

```

```


\draw
(0,0) to[vco] (1,0)
(2,0) node[mixer] (M) {}
(M.1) -- (1,0)
(M.3) to[twoport, t = $\frac{s+4}{s^2+2s+8}$] (5,0) --(6,0)
node[inputarrow] {}
(5,0) -- (5,-2) to[twoport, t = $\frac{1}{s+1}$] (2,-2) -- (M.2)
(M.1) node[inputarrow] {}
(M.2) node[inputarrow, rotate = 90]
{}
(M.1) node[anchor = west] {+}
(M.2) node[anchor = south] {+}
;
\end{circuitikz}
\end{center}

```

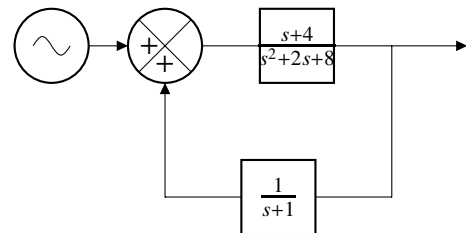
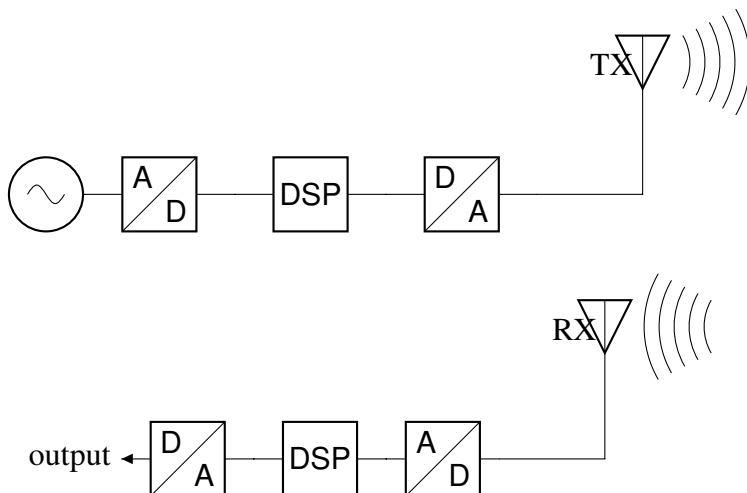
## REFERENCES

- [1] Electric Circuit Design <https://github.com/PrasannaIITH/circuitikz>



6 CONTROL SYSTEM

```

\begin{center}
\begin{circuitikz}

```